

**University of Mumbai**  
**Examination 2021 under cluster \_\_ (Lead College: \_\_\_\_\_)**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 24<sup>th</sup> June 2021**

Program: BE (Electronics and Telecommunication Engineering)

Curriculum Scheme: Revised 2016(CBCGS)

Examination: SE Semester III

Course Code: ECC301 and Course Name: Applied Mathematics-III

Time: 2 hour

Max. Marks: 80

| <b>Q1.</b> | <b>All the Questions are compulsory and carry equal marks      2 marks each</b>                         |
|------------|---|
| 1.         | Laplace Transform of $\sin(\frac{\sqrt{3}}{2}t)$ is   |
| Option A:  | $\frac{\sqrt{3}}{4s^2 + 3}$   |
| Option B:  | $\frac{2\sqrt{5}}{4s^2 + 3}$  |
| Option C:  | $\frac{2\sqrt{3}}{4s^2 + 3}$  |
| Option D:  | $\frac{2\sqrt{3}}{s^2 + 3}$   |
| 2.         | If $f(x) = 2x, 0 \leq x \leq 2\pi$ then $a_4$ is given by   |
| Option A:  | $\pi$   |
| Option B:  | $-4\pi$   |
| Option C:  | 4   |
| Option D:  | $4\pi$  |
| 3.         | What is the Fourier series expansion of the function $f(x)$ in the interval $(0, 2l)$ ?                 |
| Option A:  | $\sum_{n=1}^{\infty} a_n \cos(\frac{n\pi x}{l}) + \sum_{n=1}^{\infty} b_n \sin(\frac{n\pi x}{l})$       |
| Option B:  | $a_0 + \sum_{n=1}^{\infty} a_n \cos(\frac{n\pi x}{l})$  |
| Option C:  | $a_0 + \sum_{n=1}^{\infty} a_n \cos(\frac{n\pi x}{l}) + \sum_{n=1}^{\infty} b_n \sin(\frac{n\pi x}{l})$ |
| Option D:  | $a_0 + \sum_{n=1}^{\infty} b_n \sin(\frac{n\pi x}{l})$  |
| 4.         | Laplace Transform of $e^{3t} \sin t$ is   |
| Option A:  | $\frac{1}{(s^2 + 6s + 10)}$   |
| Option B:  | $\frac{1}{(s^2 - 6s - 10)}$   |

|           |   |
|-----------|---|
| Option C: | $\frac{3}{(s^2 - 6s + 10)}$                                   |
| Option D: | $\frac{1}{(s^2 - 6s + 10)}$                                   |
|           |   |
| 5.        | $J_{\frac{1}{2}}(x) = \dots$                                  |
| Option A: | $\sqrt{\frac{2}{\pi x}} \sin x$                               |
| Option B: | $nJ_n(x) - xJ_{n+1}(x)$                                       |
| Option C: | $nJ_n(x) + xJ_{n+1}(x)$                                       |
| Option D: | $\sqrt{\frac{2}{\pi x}} \cos x$                               |
|           |   |
| 6.        | $J_{-n}(x) = \dots$   |
| Option A: | $(-1)^n J_{n+1}(x)$   |
| Option B: | $(-1)^n J_n(x)$   |
| Option C: | $(-1)^{n+1} J_n(x)$   |
| Option D: | $(-1)J_n(x)$  |
|           |   |
| 7.        | $L^{-1}\left[\frac{s-1}{s^2-2s+5}\right] = \dots$             |
| Option A: | $e^t \cos 2t$   |
| Option B: | $e^{-t} \cos 2t$  |
| Option C: | $-e^t \cos 2t$  |
| Option D: | $e^t \cos 4t$   |
|           |   |
| 8.        | $\nabla r^n = \dots$  |
| Option A: | $nr^n r^-$  |
| Option B: | $r^{n-2} r^-$   |
| Option C: | $nr^{n+2} r^-$  |
| Option D: | $nr^{n-2} r^-$  |
|           |   |
| 9.        | The Fourier Coefficient $a_n$ for $f(x) = x^2, 0 < x < 2l$ is |
| Option A: | $-\frac{4l^2}{n^2 \pi^2}$                                     |
| Option B: | $\frac{4l^2}{n^2 \pi^2}$                                      |
| Option C: | $\frac{l^2}{n^2 \pi^2}$                                       |
| Option D: | $\frac{4l^2}{\pi^2}$  |

|           |  |
|-----------|--|
| 10.       | $\frac{d}{dx}[x^n J_n(x)] = \text{-----}$  |
| Option A: | $x^{n-1} J_{n-1}(x)$   |
| Option B: | $x^n J(x)$   |
| Option C: | $-x^n J_n(x)$  |
| Option D: | $x^n J_{n-1}(x)$   |
| 11.       | If $u = x^2 - y^2$ then analytic function $f(z)$ is  |
| Option A: | $z^2 + c$  |
| Option B: | $-z^2 + c$   |
| Option C: | $z^3 + c$  |
| Option D: | $2z^2 + c$   |
| 12.       | The only function among the following, that is analytic, is  |
| Option A: | $f(z) = R iz$  |
| Option B: | $f(z) = R m z$   |
| Option C: | $f(z) = z^-$   |
| Option D: | $f(z) = \sin z$  |
| 13.       | If $f(z)$ is analytic and equals $u(x,y) + iv(x,y)$ then $f'(z)$ equals  |
| Option A: | $\frac{\partial u}{\partial x} - i \frac{\partial u}{\partial y}$  |
| Option B: | $\frac{\partial u}{\partial x} - i \frac{\partial v}{\partial x}$  |
| Option C: | $\frac{\partial v}{\partial y} - i \frac{\partial v}{\partial x}$  |
| Option D: | $-\frac{\partial u}{\partial x} - i \frac{\partial u}{\partial y}$   |
| 14.       | Which of the following is an "even" function of $x$ ?  |
| Option A: | $\sin x$   |
| Option B: | $ x $  |
| Option C: | $x^3$  |
| Option D: | $x+1$  |
| 15.       | In a Half Range cosine series of a function which of the following Fourier coefficient is/are zero.  |
| Option A: | $a_n$  |
| Option B: | $a_0$  |
| Option C: | $b_n$  |
| Option D: | $a_0, a_n$   |
| 16.       | If a force $F = 2x^2 y i + 3xy j$ displaces a particle in the $xy$ -plane from $(0,0)$ to $(1,4)$ along a curve $y=4x^2$ then the work done is |

|            |   |
|------------|---|
| Option A:  | $\frac{104}{5}$   |
| Option B:  | $\frac{104}{25}$  |
| Option C:  | $-\frac{104}{5}$  |
| Option D:  | $\frac{10}{5}$  |
| 17.        | In order that the function $f(z) = \frac{ z ^2}{z}, z \neq 0$ be continuous at $z=0$ , we should define $f(0)$ equal to |
| Option A:  | 2   |
| Option B:  | -1  |
| Option C:  | 0   |
| Option D:  | 1   |
| 18.        | A unit normal to the surface $x^2y+2xz=4$ at the point $(2,-2,2)$ is given by   |
| Option A:  | $\frac{-i+j+k}{\sqrt{3}}$   |
| Option B:  | $\frac{i+j+k}{\sqrt{3}}$  |
| Option C:  | $\frac{-i-j+k}{\sqrt{3}}$   |
| Option D:  | $\frac{-i+j+k}{\sqrt{2}}$   |
| 19.        | A set of functions $f_1(x), f_2(x), f_3(x), \dots, f_n(x), \dots$ is said to be orthonormal if                          |
| Option A:  | $\int_a^b f_m(x)f_n(x)dx = \begin{cases} 1, & \text{if } m = n \\ 0, & \text{if } m \neq n \end{cases}$                 |
| Option B:  | $\int_a^b f_m(x)f_n(x)dx = \begin{cases} 0, & \text{if } m = n \\ 2, & \text{if } m \neq n \end{cases}$                 |
| Option C:  | $\int_a^b f_m(x)f_n(x)dx = \begin{cases} 0, & \text{if } m = n \\ 1, & \text{if } m \neq n \end{cases}$                 |
| Option D:  | $\int_a^b f_m(x)f_n(x)dx = \begin{cases} 2, & \text{if } m = n \\ 1, & \text{if } m \neq n \end{cases}$                 |
| 20.        | $L^{-1}\left[\frac{2s+3}{s^2+2s+2}\right] = \text{-----}$   |
| Option A:  | $e^{-t}(2\cos t + \sin t)$  |
| Option B:  | $e^{-t}(2\cos t - \sin t)$  |
| Option C:  | $e^{-t}(\cos t + \sin t)$   |
| Option D:  | $e^{-t}(\cos t + 2\sin t)$  |
| <b>Q2.</b> | <b>Solve any Four out of Six</b> <span style="float: right;"><b>5 marks each</b></span>                                 |

|            |   |
|------------|---|
| A          | Obtain a Fourier expression for $f(x) = x^3, -\pi < x < \pi$  |
| B          | Use Green's theorem to evaluate $\int_c (x^2 + xy)dx + (x^2 + y^2)dy$ where $c$ is the square formed by the lines $y = \pm 1, x = \pm 1$ .                                  |
| C          | Find the Laplace Transform of the Periodic function<br>$f(t) = \frac{kt}{T}, 0 < t < T, f(t+T) = f(t)$  |
| D          | Let $f(z) = u(r, \theta) + iv(r, \theta)$ be an analytic function. If $u = -r^3 \sin 3\theta$ then construct the corresponding analytic function $f(z)$ in terms of $z$ .   |
| E          | Find the value of 'n' for which the vector $r^n r^-$ is solenoidal, where $r^- = xi + yj + zk$  |
| F          | Solve the initial value problem $2 \frac{d^2 y}{dt^2} + 5 \frac{dy}{dt} + 2y = e^{-2t}, y(0) = 1, y'(0) = 1$  |
| <b>Q3.</b> | <b>Solve any Four out of Six</b> <span style="float: right;"><b>5 marks each</b></span>   |
| A          | Using the convolution theorem, find $L^{-1}[\frac{s^2}{(s^2 + a^2)(s^2 + b^2)}], a \neq b$  |
| B          | A fluid motion is given by<br>$v^- = (y \sin z - \sin x)i + (x \sin z + 2yz)j + (xy \cos z + y^2)k$ is the motion irrotational? If so, find the velocity potential.         |
| C          | Evaluate $L[\frac{e^{-4t} \sin 3t}{t}]$   |
| D          | Find the image of $ z - 3i  = 3$ under the mapping $w = \frac{1}{z}$  |
| E          | Using Stoke's theorem, evaluate $\int_c [(2x - y)dx - yz^2 dy - y^2 z dz]$ where $c$ is the circle $x^2 + y^2 = 1$ , corresponding to the surface of sphere of unit radius. |
| F          | Given that $f(x) = x + x^2, -\pi < x < \pi$ , find the Fourier expression of $f(x)$   |

**University of Mumbai**  
**Examination 2021 under cluster \_\_ (Lead College: \_\_\_\_\_)**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 24<sup>th</sup> June 2021**

Program: BE (Electronics and Telecommunication Engineering)

Curriculum Scheme: Revised 2016(CBCGS)

Examination: Second Year Semester III

Course Code: ECC301 and Course Name: Applied Mathematics-III

Time: 2 hour

Max. Marks: 80

---

| Question Number | Correct Option<br>(Enter either 'A' or 'B' or 'C' or 'D') |
|-----------------|---|
| Q1.             | C   |
| Q2.             | D   |
| Q3.             | C   |
| Q4              | D   |
| Q5              | A   |
| Q6              | B   |
| Q7              | A   |
| Q8.             | D   |
| Q9.             | B   |
| Q10.            | D   |
| Q11.            | A   |
| Q12.            | D   |
| Q13.            | C   |
| Q14.            | B   |
| Q15.            | C   |
| Q16.            | A   |
| Q17.            | C   |
| Q18.            | A   |
| Q19.            | C   |
| Q20.            | A   |

# University of Mumbai

Examination June 2021

Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021

Program: Electronics and Telecommunication Engineering

Curriculum Scheme: Rev-2016

Examination: SE Semester III

Course Code: ECC304 and Course Name: Circuit Theory and Network

Time: 2 Hour

Max. Marks: 80

|            |  |
|------------|--|
| <b>Q1.</b> | <b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b>     |
| 1.         | Laplace equivalent of Inductor(L) with zero initial condition is given by ----.                                      |
| Option A:  | 1/L  |
| Option B:  | LS   |
| Option C:  | 1/LS   |
| Option D:  | L/S  |
| 2.         | Find $V_x$   |
| Option A:  | 6 V  |
| Option B:  | 2 V  |
| Option C:  | 7 V  |
| Option D:  | 9 V  |
| 3.         | In nodal analysis, if there are 6 nodes in the circuit then how many equations will be written to solve the network? |
| Option A:  | 7  |
| Option B:  | 6  |
| Option C:  | 5  |
| Option D:  | 4  |
| 4.         | The Thevenin voltage at terminal A-B is  |
| Option A:  | 9.6 V  |
| Option B:  | 2.5 V  |
| Option C:  | 14.5 V   |

|           |  |
|-----------|--|
| Option D: | 15 V   |
|           |  |
| 5.        | Find current $I_x$ .   |
|           |  |
| Option A: | 2 A  |
| Option B: | 0.25 A   |
| Option C: | 0.50 A   |
| Option D: | 0.17 A   |
|           |  |
| 6.        | How many tie sets will be generated for a graph with 4 nodes and 5 branches?   |
| Option A: | 2  |
| Option B: | 5  |
| Option C: | 7  |
| Option D: | 3  |
|           |  |
| 7.        | If Y-parameters are $Y_{11} = 0.5$ , $Y_{22} = 1$ and $Y_{12} = Y_{21} = -0.2$ , what would be the value of $\Delta Y$ .           |
| Option A: | 2  |
| Option B: | 3  |
| Option C: | 0.32   |
| Option D: | 0.46   |
|           |  |
| 8.        | Reverse voltage gain with output port open circuited in Transmission-parameters is a unitless quantity and generally equivalent to |
| Option A: | $V_1 / I_1$ (keeping $V_2 = 0$ )   |
| Option B: | $I_2 / I_1$ (keeping $V_2 = 0$ )   |
| Option C: | $V_1 / V_2$ (keeping $I_2 = 0$ )   |
| Option D: | $I_2 / V_2$ (keeping $I_1 = 0$ )   |
|           |  |
| 9.        | In the following RC series circuit, switch is closed at $t=0$ , Find $i(o+)$ .   |
|           |  |
| Option A: | 0.1 A  |
| Option B: | 0.2 A  |
| Option C: | 0.3 A  |
| Option D: | 2 A  |
|           |  |
| 10.       | Find $I_2 / I_1$   |
|           |  |



|           |  |
|-----------|--|
|           |  |
| Option A: | $200/(S^2+20S+400)$  |
| Option B: | $S/(S+2)$  |
| Option C: | $400/(S^2+20S+400)$  |
| Option D: | $(S+4)/S(S+1)$   |
|           |  |
| 11.       | Superposition theorem is not applicable to network containing  |
| Option A: | Nonlinear element  |
| Option B: | Linear element   |
| Option C: | Dependent current source   |
| Option D: | Dependent voltage source   |
|           |  |
| 12.       | Find $Z_{11}$ for the network  |
|           |  |
| Option A: | 3  |
| Option B: | 2  |
| Option C: | 4  |
| Option D: | 5  |
|           |  |
| 13.       | In which properties of realization of function is that Highest as well as lowest power of Numerator and denominator differ by unity. |
| Option A: | RC   |
| Option B: | LC   |
| Option C: | RL   |
| Option D: | RLC  |
|           |  |
| 14.       | A 2-port network is shown in the figure. The parameter $h_{21}$ for this network can be given by                                     |
|           |  |
| Option A: | -0.5   |
| Option B: | -0.25  |
| Option C: | -2   |
| Option D: | -4.5   |
|           |  |
| 15.       | In the network, switch is closed and a steady state is reached in network, At $t=0$ , switch is opened, Find $i_2(0^-)$              |

|           |   |
|-----------|---|
|           |   |
| Option A: | 10 A  |
| Option B: | 20 A  |
| Option C: | 30 A  |
| Option D: | 40 A  |
|           |   |
| 16.       | Find voltage transfer function $V_2(S)/V_1(S)$ of two port network. |
|           |   |
| Option A: | $1/(RCS+1)$   |
| Option B: | $R+CS$  |
| Option C: | $RCS+1$   |
| Option D: | $R/CS$  |
|           |   |
| 17.       | The driving point impedance function $Z(S)$ of the network is       |
|           |   |
| Option A: | $(20S^4+22S^2+1)/5S(3S^2+1)$  |
| Option B: | $(30S^4+S^2+1)/5S(2S^2+1)$  |
| Option C: | $1.5(S+2)/S+1.5$  |
| Option D: | $(30S^4+22S^2+1)/5S(2S^2+1)$  |
|           |   |
| 18.       | Assume zero voltage across capacitor at $t=0$ , $i(0^+)$ is         |
|           |   |
| Option A: | 20 A  |
| Option B: | 50A   |
| Option C: | 30 A  |
| Option D: | 40 A  |
|           |   |
| 19.       | Which of following is not Hurwitz polynomial?                       |
| Option A: | $S^4+4S^3+5S+1$   |
| Option B: | $S^5+ S^4+4S^3+5S+8$  |

|           |   |
|-----------|---|
| Option C: | $(S+1)(S^2+2S+3)$   |
| Option D: | $S^5+ S^4+4S^3-5S+1$  |
| 20.       | Which of following positive real function $F(S)$ , residue test is carried out? |
| Option A: | $(S+3)/(S+1)$   |
| Option B: | $(S^2+1)/(S^3+4S)$  |
| Option C: | $(S^3+6S^2+7S+3)/(S^2+2S+1)$  |
| Option D: | $(S^2+6S+5)/(S^2+9S+14)$  |

### subjective/descriptive questions

| <b>Q2</b> | <b>Solve any Two Questions out of Three</b>   | <b>10 marks each</b> |
|-----------|---|----------------------|
| A         | Find Nortons equivalent network at terminal A and B   |                      |
| B         | For the network shown, determine $Z_{11}(S)$ , $G_{12}(S)$ and $Z_{12}(S)$ .                              |                      |
| C         | Two Identical sections of network are connected in cascade, obtain ABCD Parameters of overall connections |                      |

| <b>Q3.</b> | <b>Solve any Two Questions out of Three</b>               | <b>10 marks each</b> |
|------------|---|----------------------|
| A          | Obtain equilibrium equation on node basis for the network |                      |

|   |   |
|---|---|
|   |   |
| B | <b>In the Network, switch is closed, assuming all initial conditions as zero, Find <math>i, di/dt, d^2i/dt^2</math></b>     |
| C | <b>Realize Impedance function in Foster I and Foster II form.</b><br><br><b><math>Z(s) = S(S^2+4)/(S^2+1)(S^2+9)</math></b> |

**University of Mumbai**

**Examination June 2021**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021**

Program: Electronics and Telecommunication Engineering

Curriculum Scheme: Rev-2016

Examination: Second Year Semester III

Course Code: ECC304 and Course Name: Circuit Theory and Network

Time: 2 hour

Max. Marks: 80

| Question Number | Correct Option<br>(Enter either 'A' or 'B' or 'C' or 'D') |
|-----------------|---|
| Q1.             | B   |
| Q2.             | A   |
| Q3.             | C   |
| Q4              | A   |
| Q5              | B   |
| Q6              | A   |
| Q7              | D   |
| Q8.             | C   |
| Q9.             | A   |
| Q10.            | C   |
| Q11.            | A   |
| Q12.            | A   |
| Q13.            | B   |
| Q14.            | A   |
| Q15.            | A   |
| Q16.            | A   |
| Q17.            | D   |
| Q18.            | B   |
| Q19.            | D   |
| Q20.            | B   |

# University of Mumbai

Examination June 2021

Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021

Program: BE Electronics and Telecommunication

Curriculum Scheme: Rev2016

Examination: SE Semester III

Course Code: ECC303 and Course Name: Digital System Design

Time: 2 hour

Max. Marks: 80

|            |  |
|------------|--|
| <b>Q1.</b> | <b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks</b> |
| 1.         | The representation of octal number (531.2) <sub>8</sub> in decimal is  |
| Option A:  | (346.25) <sub>10</sub>   |
| Option B:  | (532.864) <sub>10</sub>  |
| Option C:  | (345.25) <sub>10</sub>   |
| Option D:  | (531.668) <sub>10</sub>  |
| 2.         | Representation of hexadecimal number (6FC) <sub>H</sub> in decimal:  |
| Option A:  | $6 * 16^2 + 13 * 16^1 + 14 * 16^0$   |
| Option B:  | $6 * 16^2 + 15 * 16^1 + 12 * 16^0$   |
| Option C:  | $6 * 16^2 + 12 * 16^1 + 13 * 16^0$   |
| Option D:  | $6 * 16^2 + 14 * 16^1 + 15 * 16^0$   |
| 3.         | 2's complement of 10101011 is _____  |
| Option A:  | 01010101   |
| Option B:  | 11010100   |
| Option C:  | 00110101   |
| Option D:  | 11100010   |
| 4.         | On subtracting (01010) <sub>2</sub> from (11100) <sub>2</sub> using 1's complement, we get _____.                |
| Option A:  | 01001  |
| Option B:  | 10010  |
| Option C:  | 10101  |
| Option D:  | 10100  |
| 5.         | How many truth table entries are necessary for a three-input circuit?  |
| Option A:  | 4  |
| Option B:  | 12   |
| Option C:  | 8  |
| Option D:  | 16   |
| 6.         | Which input values will cause an AND logic gate to produce a HIGH output?  |
| Option A:  | At least one input is HIGH   |
| Option B:  | At least one input is LOW  |
| Option C:  | All inputs are HIGH  |
| Option D:  | All inputs are LOW   |

|           |  |
|-----------|--|
| 7.        | Exclusive-OR (XOR) logic gates can be constructed from what other logic gates?       |
| Option A: | AND gates, OR gates, and NOT gates   |
| Option B: | OR gates only  |
| Option C: | OR gates and NOT gates   |
| Option D: | AND gates and NOT gates  |
| 8.        | Transistor-transistor logic (TTL) is a class of digital circuits built from _____.   |
| Option A: | JFET only  |
| Option B: | Bipolar junction transistors (BJT)   |
| Option C: | Resistors  |
| Option D: | Bipolar junction transistors (BJT) and resistors                                     |
| 9.        | TTL devices consume substantially _____ power than equivalent CMOS devices at rest.  |
| Option A: | Less   |
| Option B: | More   |
| Option C: | Equal  |
| Option D: | Very High  |
| 10.       | CMOS technology is used in _____.  |
| Option A: | Inverter   |
| Option B: | Microprocessor   |
| Option C: | Digital logic  |
| Option D: | Both microprocessor and digital logic  |
| 11.       | One application of an S-R flip-flop is as _____.                                     |
| Option A: | Transition pulse generator   |
| Option B: | Racer  |
| Option C: | Switch debouncer   |
| Option D: | Astable oscillator   |
| 12.       | The truth table for an S-R flip-flop has how many VALID entries?                     |
| Option A: | 1  |
| Option B: | 2  |
| Option C: | 3  |
| Option D: | 4  |
| 13.       | What is a trigger pulse?   |
| Option A: | A pulse that starts a cycle of operation   |
| Option B: | A pulse that reverses the cycle of operation   |
| Option C: | A pulse that prevents a cycle of operation   |
| Option D: | A pulse that enhances a cycle of operation   |
| 14.       | A counter circuit is usually constructed of _____.                                   |
| Option A: | A number of latches connected in cascade form  |
| Option B: | A number of NAND gates connected in cascade form                                     |
| Option C: | A number of flip-flops connected in cascade  |
| Option D: | A number of NOR gates connected in cascade form                                      |
| 15.       | Which one of the following has capability to store data in extremely high densities? |

|           |   |
|-----------|---|
| Option A: | Register  |
| Option B: | Capacitor   |
| Option C: | Semiconductor   |
| Option D: | Flip-Flop   |
| 16.       | A shift register that will accept a parallel input or a bidirectional serial load and internal shift features is called as?                                   |
| Option A: | Tristate  |
| Option B: | End around  |
| Option C: | Universal   |
| Option D: | Conversion  |
| 17.       | A 5-bit asynchronous binary counter is made up of five flip-flops, each with a 12 ns propagation delay. The total propagation delay ( $t_{p(tot)}$ ) is _____ |
| Option A: | 12 ms   |
| Option B: | 24 ns   |
| Option C: | 48 ns   |
| Option D: | 60 ns   |
| 18.       | Which is not a type of shift register?  |
| Option A: | Serial in/parallel in   |
| Option B: | Serial in/parallel out  |
| Option C: | Parallel in/serial out  |
| Option D: | Parallel in/parallel out  |
| 19.       | Which of the following is not a type of VHDL modeling?  |
| Option A: | Behavioral modeling   |
| Option B: | Dataflow modeling   |
| Option C: | Structural modeling   |
| Option D: | Component modeling  |
| 20.       | The difference between a PAL & a PLA is _____   |
| Option A: | PALs and PLAs are the same thing  |
| Option B: | The PLA has a programmable OR plane and a programmable AND plane, while the PAL only has a programmable AND plane   |
| Option C: | The PAL has a programmable OR plane and a programmable AND plane, while the PLA only has a programmable AND plane   |
| Option D: | The PAL has more possible product terms than the PLA  |

|                                     |                                  |                     |
|-------------------------------------|----------------------------------|---------------------|
| <b>Q2</b><br><b>(20 Marks Each)</b> | <b>Solve any Four out of Six</b> | <b>5 marks each</b> |
| A                                   | Write a short note on Gray code. |                     |
| B                                   | Write a short note on VHDL.      |                     |



|   |  |
|---|--|
| C | Explain carry look ahead adder with necessary diagram. |
| D | Explain Master-Slave JK flip-flop.                     |
| E | Explain Flash memories.                                |
| F | Differentiate between Moore and Mealy circuits.        |

|                                      |   |
|--------------------------------------|---|
| <b>Q3.</b><br><b>(20 Marks Each)</b> | <b>Solve any Four out of Six</b><br><b>5 marks each</b> |
| A                                    | Explain De-Morgan's theorems and prove it.              |
| B                                    | Compare TTL and CMOS logic families.                    |
| C                                    | Convert J-K flip flop to T flip flop.                   |
| D                                    | Differentiate between PAL and PLA.                      |
| E                                    | Explain Johnson's counter.                              |
| F                                    | Design 16:1 multiplexer using 4:1 multiplexer.          |

**University of Mumbai**

**Examination June 2021**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021**

Program: BE Electronics and Telecommunication

Curriculum Scheme: Rev2016

Examination: SE Semester III

Course Code: ECC303 and Course Name: Digital System Design

Time: 2 hour

Max. Marks: 80

---

| Question Number | Correct Option<br>(Enter either 'A' or 'B' or 'C' or 'D') |
|-----------------|---|
| Q1.             | C   |
| Q2.             | B   |
| Q3.             | A   |
| Q4              | B   |
| Q5              | C   |
| Q6              | C   |
| Q7              | A   |
| Q8.             | D   |
| Q9.             | B   |
| Q10.            | D   |
| Q11.            | C   |
| Q12.            | C   |
| Q13.            | A   |
| Q14.            | C   |
| Q15.            | C   |
| Q16.            | C   |
| Q17.            | D   |
| Q18.            | A   |
| Q19.            | D   |
| Q20.            | B   |

# University of Mumbai

Examination June 2021

Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021

Program: **Electronics & Telecommunication**

Curriculum Scheme: Rev 2016

Examination: SE Semester III

Course Code: ECC302 and Course Name: Electronic Devices & Circuits-I


Time: 2 hour


Max. Marks: 80

|            |   |
|------------|---|
| <b>Q1.</b> | <b>Choose the correct option for following questions. All the Questions are compulsory and carry equal marks.</b>   |
| 1.         | Gain bandwidth product is a transistor parameter that is constant and equal to ____.  |
| Option A:  | Total frequency   |
| Option B:  | Unity gain frequency  |
| Option C:  | Sum of frequencies  |
| Option D:  | Critical frequency  |
| 2.         | A capacitor having rating 50 $\mu$ F, 6V and plus sign near to one of its terminals, the capacitor must be ____.  |
| Option A:  | A mica capacitor  |
| Option B:  | A ceramic capacitor   |
| Option C:  | An electrolytic capacitor   |
| Option D:  | An Air Gang capacitor   |
| 3.         | In a LC filter, the ripple factor ____.   |
| Option A:  | Increases with the load current   |
| Option B:  | increases with the load resistance  |
| Option C:  | remains constant with the load current  |
| Option D:  | has the lowest value  |
| 4.         | The input impedance of a FET is of the order of ____.   |
| Option A:  | $10^2$ ohms   |
| Option B:  | Hundreds of Mega ohms   |
| Option C:  | Hundred ohms  |
| Option D:  | A few ohms  |
| 5.         | In designing a CS JFET amplifier, which of the data is not provided by the datasheet?   |
| Option A:  | Transconductance ( $g_{m0}$ )   |
| Option B:  | Pinch off voltage   |
| Option C:  | Voltage gain  |
| Option D:  | $I_{DSS}$   |
| 6.         | A bipolar transistor is operating in the active region with a collector current of 1 mA. Assuming that the $\beta$ of the transistor is 100 and the thermal voltage ( $V_T$ ) is 25 mV. The transconductance and the input resistance ( $r_{\pi}$ ) of the transistor in the common emitter configuration are |

|           |  |
|-----------|--|
| Option A: | $g_m = 25 \text{ mA/V}$ and $r_{\pi} = 15.625 \text{ k}\Omega$   |
| Option B: | $g_m = 40 \text{ mA/V}$ and $r_{\pi} = 4 \text{ k}\Omega$  |
| Option C: | $g_m = 25 \text{ mA/V}$ and $r_{\pi} = 2.5 \text{ k}\Omega$  |
| Option D: | $g_m = 40 \text{ mA/V}$ and $r_{\pi} = 2.5 \text{ k}\Omega$  |
|           |  |
| 7.        | For which of the following conditions the designing of the JFET amplifier cannot be done?  |
| Option A: | Midpoint Biasing   |
| Option B: | Variation in $I_{DS}$  |
| Option C: | Zero temperature drift   |
| Option D: | Variation in beta parameter  |
|           |  |
| 8.        | For a CE amplifier with voltage divider biasing with bypassed $R_E$ , $R_1 = 40 \text{ k}\Omega$ , $R_2 = 10 \text{ k}\Omega$ , $r_{\pi} = 1.15 \text{ k}\Omega$ the input impedance of the amplifier using hybrid pi model is |
| Option A: | $1.005 \text{ k}\Omega$  |
| Option B: | $9.15 \text{ k}\Omega$   |
| Option C: | $5.15 \text{ k}\Omega$   |
| Option D: | $8.25 \text{ k}\Omega$   |
|           |  |
| 9.        | The % load regulation of a power supply should be ideally _____ & practically _____  |
| Option A: | zero, small  |
| Option B: | small, zero  |
| Option C: | zero, large  |
| Option D: | large, zero  |
|           |  |
| 10.       | In a common-source JFET amplifier, the output voltage is .....   |
| Option A: | $180^\circ$ out of phase with the input  |
| Option B: | in phase with the input  |
| Option C: | $90^\circ$ out of phase with the input   |
| Option D: | taken at the source  |
|           |  |
| 11.       | For a self-bias circuit, find drain to source voltage if $V_{DD}=12\text{V}$ , $I_D=1\text{mA}$ , $R_s=R_D=1\text{K}\Omega$ ?  |
| Option A: | 1 V  |
| Option B: | 2 V  |
| Option C: | 10 V   |
| Option D: | 5 V  |
|           |  |
| 12.       | Generally, the gain of a transistor amplifier falls at high frequency due to the   |
| Option A: | Internal capacitance of the device   |
| Option B: | Coupling capacitor at the input  |
| Option C: | Skin effect  |
| Option D: | Coupling capacitor at the output   |
|           |  |
| 13.       | For design of self-bias CS JFET circuit, if the lower cut of frequency is $20 \text{ Hz}$ , $R_G$ is $1 \text{ M}\Omega$ then the value of input coupling capacitor is ____ .  |
| Option A: | $8 \text{ nF}$   |
| Option B: | $80 \text{ nF}$  |

|           |   |
|-----------|---|
| Option C: | 8 $\mu\text{F}$   |
| Option D: | 80 $\mu\text{F}$  |
| 14.       | In a small signal equivalent model of an FET, what does $g_m V_{GS}$ stand for?   |
| Option A: | A pure resistor   |
| Option B: | Voltage controlled current source   |
| Option C: | Current controlled current source   |
| Option D: | Voltage controlled voltage source   |
| 15.       | Which resistance in the hybrid $\pi$ model of transistor represents the bulk resistance present between the external base terminal and the virtual base?  |
| Option A: | Collector-to-emitter resistance ( $r_{ce}$ )  |
| Option B: | Base spreading resistance ( $r_{bb}$ )  |
| Option C: | Virtual base to emitter resistance ( $r_{be}$ )   |
| Option D: | Emitter resistance ( $R_E$ )  |
| 16.       | In voltage divider bias, $V_{CC} = 25 \text{ V}$ ; $R_1 = 10 \text{ k}\Omega$ ; $R_2 = 5 \text{ k}\Omega$ ; $V_{BE} = 0.7 \text{ V}$ , $R_C = 2 \text{ k}\Omega$ , $\beta = 100$ and $R_E = 1 \text{ k}\Omega$ . What is the emitter voltage? |
| Option A: | 3.71 V  |
| Option B: | 5.35 V  |
| Option C: | 4.96V   |
| Option D: | 7.38 V  |
| 17.       | If $R_C$ and $R_L$ represent the collector resistance and load resistance respectively in a single stage transistor amplifier, then a.c. load is .....  |
| Option A: | $R_L + R_C$   |
| Option B: | $R_C \parallel R_L$   |
| Option C: | $R_L - R_C$   |
| Option D: | $R_C$   |
| 18.       | In a shunt capacitor filter, the mechanism that helps the removal of ripples is _____.  |
| Option A: | The current passing through the capacitor   |
| Option B: | The voltage variations produced by shunting the capacitor   |
| Option C: | The property of capacitor to store electrical energy  |
| Option D: | Uniform charge flow through the rectifier   |
| 19.       | Which effect plays a critical role in producing changes in the frequency response of the BJT.?  |
| Option A: | Thevenin's effect   |
| Option B: | Miller effect   |
| Option C: | Tellegen's effect   |
| Option D: | Norton's effect   |
| 20.       | Zener diode is designed to specifically work in which region without getting damaged?   |
| Option A: | Active region   |
| Option B: | Breakdown region  |
| Option C: | Forward bias  |
| Option D: | Reverse bias  |
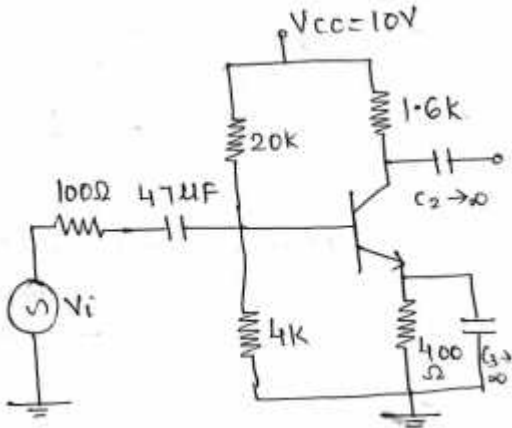
| Q2 | Solve any Two Questions out of Three   | 10 marks each |
|----|--|---------------|
| A  | Design the resistors for a single stage RC coupled CE amplifier to meet the following specifications $V_o=2V$ , $A_v=90$ , $S=8$ , $f_L=20$ Hz.  |               |
| B  | Draw a neat circuit diagram of CS FET amplifier and derive the expression for input impedance, output impedance and voltage gain.  |               |
| C  | <p>For the circuit shown below, the transistor parameters are <math>V_{BE(on)} = 0.7</math> V, <math>\beta = 100</math>, find the lower cut off frequency of the circuit.</p>  |               |
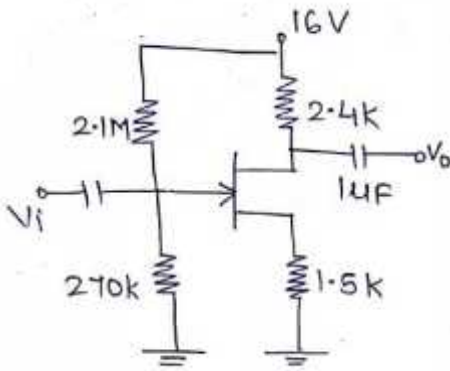
| Q3 | Solve any Two Questions out of Three  | 10 marks each |
|----|---|---------------|
| A  | <p>For the circuit shown below, <math>I_{DSS} = 8 \text{ mA}</math>, <math>V_P = -4 \text{ V}</math>, determine <math>V_{GS}</math>, <math>V_{DS}</math> and <math>I_D</math></p>  |               |
| B  | A full wave rectifier with center tapped transformer and 2 diodes gives dc output voltage at 18 V to a resistive load and a current of $75 \pm 25 \text{ mA}$ . If ripple factor is to be 0.06 design an inductor filter.   |               |
| C  | Define stability factor. Derive the equation for stability factor. State which biasing technique is more stable. Justify your answer.   |               |

**University of Mumbai**

**Examination June 2021**

**Examinations Commencing from 15<sup>th</sup> June 2021 to 26<sup>th</sup> June 2021**

**Program: Electronics & Telecommunication**

Curriculum Scheme: Rev 2016

Examination: SE Semester III

Course Code: ECC302 and Course Name: Electronic Devices & Circuits-I

Time: 2 hour

Max. Marks: 80

=====

| Question Number | Correct Option |
|-----------------|----------------|
| Q1.             | B              |
| Q2.             | C              |
| Q3.             | C              |
| Q4              | B              |
| Q5              | C              |
| Q6              | D              |
| Q7              | D              |
| Q8.             | A              |
| Q9.             | A              |
| Q10.            | A              |
| Q11.            | C              |
| Q12.            | A              |
| Q13.            | A              |
| Q14.            | B              |
| Q15.            | B              |
| Q16.            | D              |
| Q17.            | B              |
| Q18.            | C              |
| Q19.            | B              |
| Q20.            | B              |