

University of Mumbai

Sample Question paper

Program: **Electronics Engineering**


Curriculum Scheme: Rev2019



Examination: SE Semester III

Course Code: ELC304 and Course Name:ENAS


Time: 2 hour

Max. Marks: 80

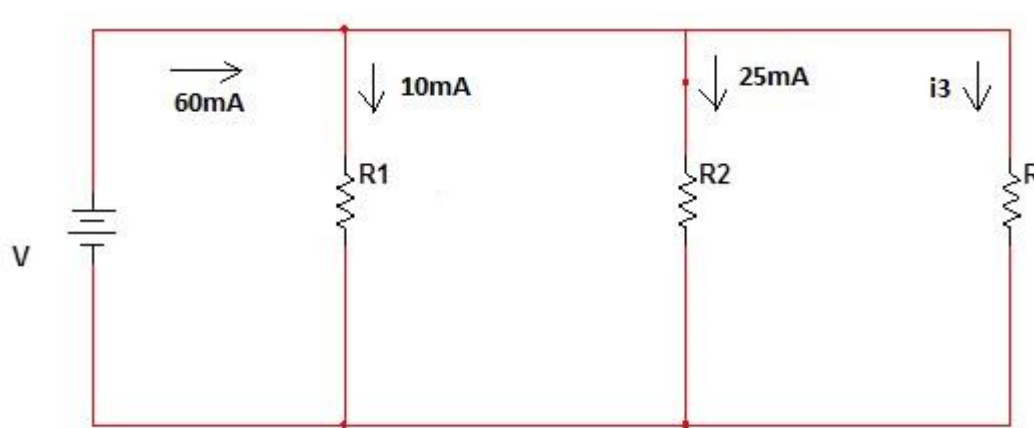Q1. (40 Marks)	Choose the correct option for following questions. All the Questions are compulsory and carry equal marks
Q1.	Which is the condition of symmetry for h parameters
Option A:	$h_{12} = -h_{21}$
Option B:	$h_{11}h_{22} - h_{12}h_{21} = 1$
Option C:	$h_{11}h_{21} - h_{12}h_{22} = 1$
Option D:	$h_{11} = 22$
Q2.	A $25\ \Omega$ resistor has a voltage of $150 \sin 377 t$. Find the corresponding power.
Option A:	$900 \sin^2 377 t$
Option B:	$90 \sin^2 377 t$
Option C:	$900 \sin^2 377 t$
Option D:	$9 \sin^2 377 t$
Q3.	 Determine the current through the resistor R3 shown in the figure using KCL
Option A:	25mA

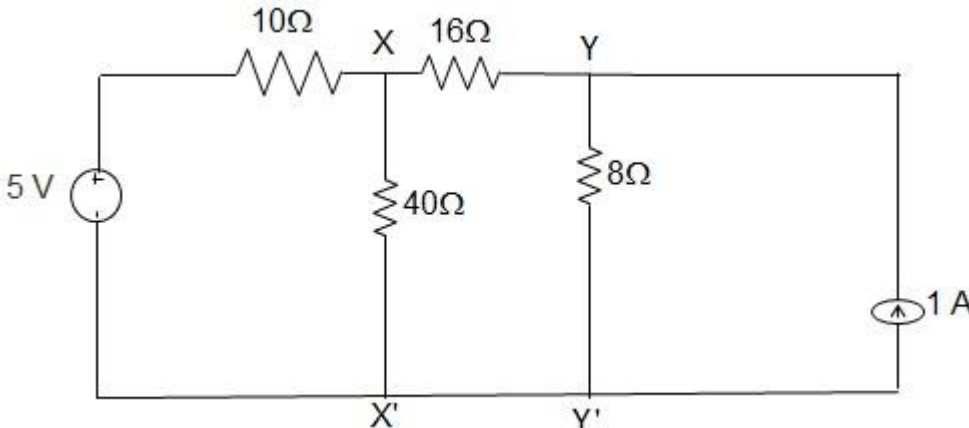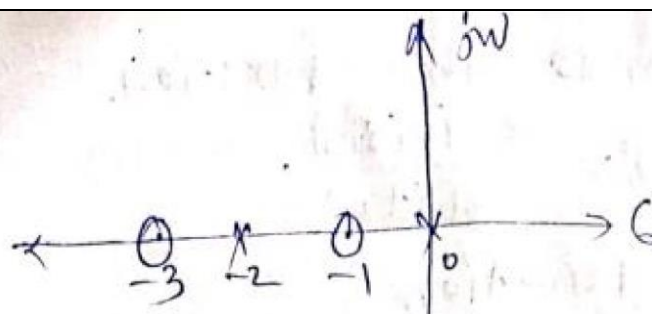Option B:	10mA
Option C:	20mA
Option D:	35mA
Q4.	A circuit is given in the figure below. The Thevenin equivalent as viewed from terminals x and x' is
	
Option A:	8 V and 6 Ω
Option B:	5 V and 6 Ω
Option C:	5 V and 32 Ω
Option D:	8 V and 32 Ω
Q5.	 Which is this function network. (a) RL network . (b) RC network (c) LC network (d) RLC network .
Option A:	
Option B:	
Option C:	
Option D:	

Q6.

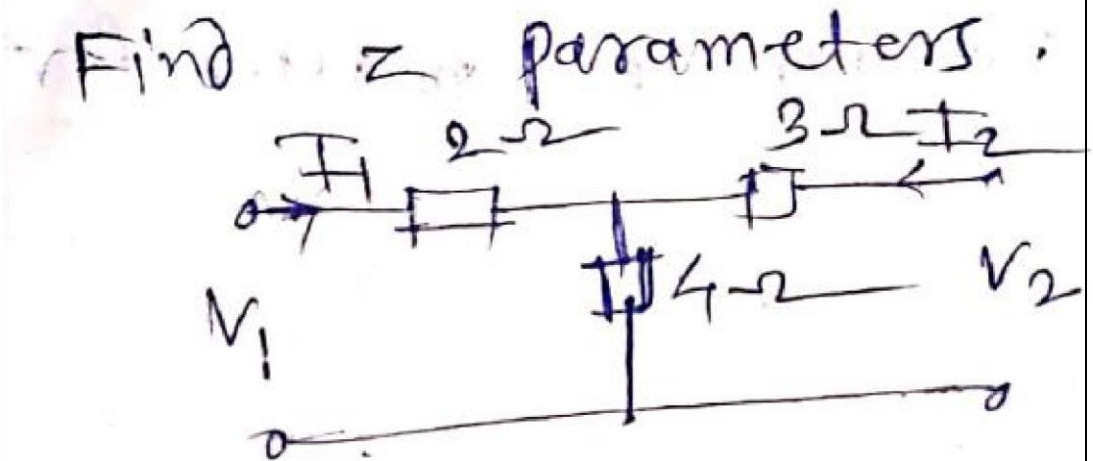

(a) $\begin{bmatrix} 6 & 4 \\ 4 & 7 \end{bmatrix}$

(b) $\begin{bmatrix} 4 & 6 \\ 6 & 7 \end{bmatrix}$

(c) $\begin{bmatrix} 4 & 6 \\ 4 & 6 \end{bmatrix}$

(d) $\begin{bmatrix} 6 & 4 \\ 7 & 4 \end{bmatrix}$

Option A:

Option B:



Option C:



Option D:



Q7.

In the following circuit, when $R = 0 \Omega$, the current I_R equals to 10 A. The maximum power will be?

Option A:	50 W
Option B:	100 W
Option C:	200 W
Option D:	400 W
Q8.	. Find the voltage (V) at node 3 in the figure shown below.
Option A:	18
Option B:	20
Option C:	22
Option D:	24
Q9.	The circuit shown in figure has a load equivalent to _____
Option A:	4 Ω

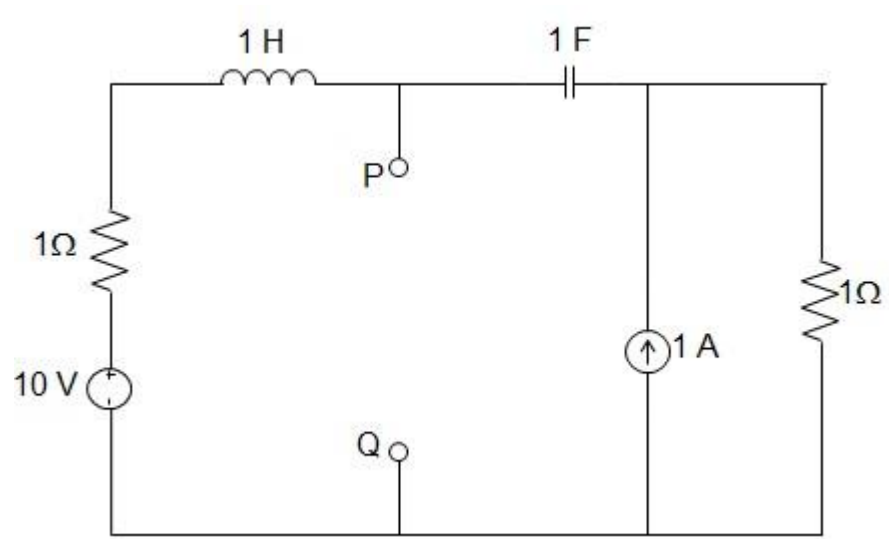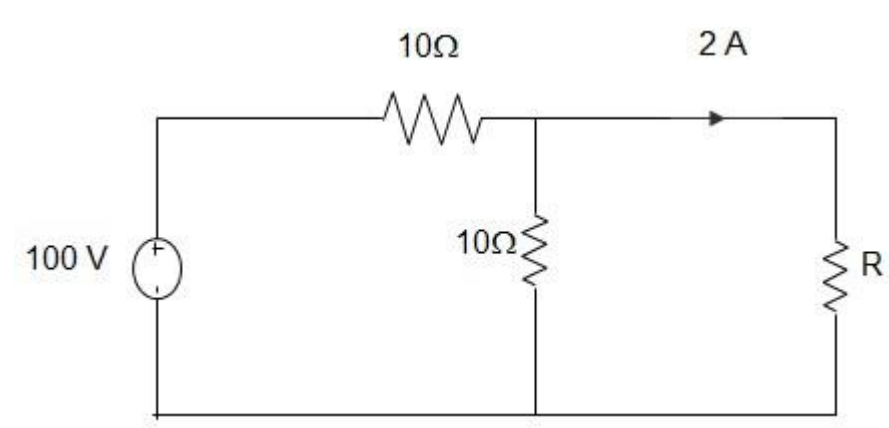Option B:	$\frac{3}{8} \Omega$
Option C:	4Ω
Option D:	3Ω
Q10.	The Norton equivalent impedance Z between the nodes P and Q in the following circuit is _____ 
Option A:	1
Option B:	$1 + s + 1/s$
Option C:	$2 + s + 1/s$
Option D:	$3 + s + 1/s$
Q11.	In the figure given below, the value of Resistance R by Superposition Theorem is _____ 
Option A:	10
Option B:	20
Option C:	30
Option D:	40


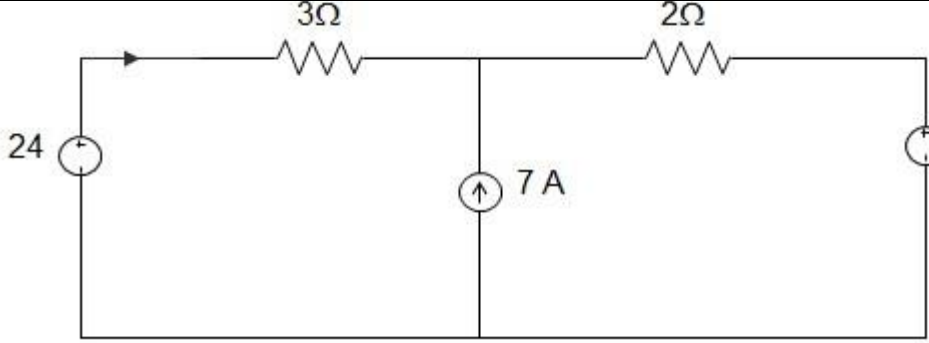
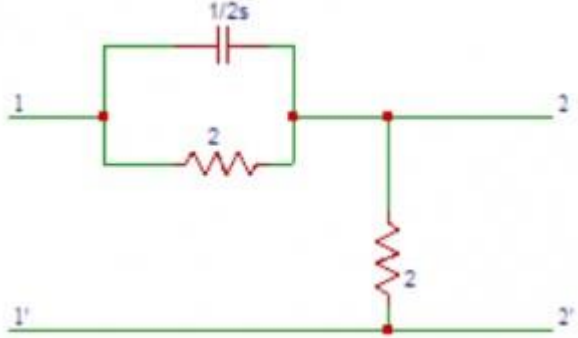
Q12.	The current I in the circuit given below is _____
	
Option A:	$\frac{1}{4}$
Option B:	$\frac{5}{4}$
Option C:	$\frac{3}{4}$
Option D:	$\frac{1}{2}$
Q13.	The unit step is not defined at $t = ?$
Option A:	0
Option B:	1
Option C:	2
Q14.	 For the network shown in the figure, find the driving point impedance.
Option A:	$(s^2 - 2s + 1)/s$
Option B:	$(s^2 + 2s + 1)/s$
Option C:	$(s^2 - 2s - 1)/s$
Option D:	$(s^2 + 2s - 1)/s$
Q15.	 Obtain the transfer function $G_{21}(s)$ in the circuit shown below.
Option A:	$(8s + 2)/(8s + 1)$
Option B:	$(8s + 2)/(8s + 2)$

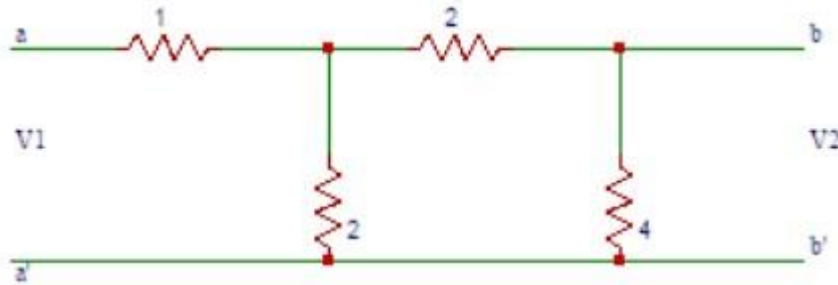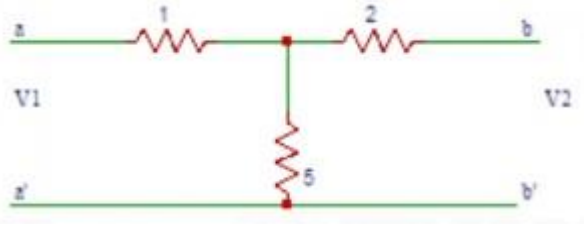Option C:	$(8S+2)/(8S+3)$
Option D:	$(8S+2)/(8S+4)$
Q16.	Which of the following expression is true in case of open circuit parameters?
Option A:	$V_2 = Z_{21}I_1 + Z_{22}I_2$
Option B:	$V_2 = Z_{21}I_1 + Z_{22}I_2$
Option C:	$V_1 = Z_{21}I_2 + Z_{22}I_2$
Option D:	$V_1 = Z_{21}I_1 + Z_{22}I_2$
Q17.	 Find the Z – parameter Z_{11} in the circuit shown below.
Option A:	1
Option B:	1.5
Option C:	2
Option D:	2.5
Option A:	1
Q18.	Which of the following expression is true in case of short circuit parameters?
Option A:	$I_2 = Y_{21}I_1 + Y_{22}I_2$
Option B:	$V_2 = Y_{21}I_1 + Y_{22}V_2$
Option C:	$I_2 = Y_{21}V_1 + Y_{22}V_2$
Option D:	$I_2 = Y_{21}V_1 + Y_{22}I_2$
Q19.	 .In the circuit shown below, find the transmission parameter A.
Option A:	6/5
Option B:	5/6
Option C:	$\frac{3}{4}$
Option D:	$\frac{4}{3}$
Q20.	The hybrid parameter h_{21} is called?
Option A:	open circuit output admittance

Option B:	open circuit reverse voltage gain
Option C:	short circuit forward current gain
Option D:	short circuit input impedance

Q2.	
A	Solve any Two 5 marks each
i.	Find the equivalent Inductance of the Network
ii.	Synthesis in Cauer II $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$
iii.	Synthesis in Cauer I $Z(s) = \frac{(s^2+1)(s^2+9)}{s(s^2+4)}$
B	Solve any One 10 marks each
i.	In the network, determine currents $i_1(t)$ and $i_2(t)$ when the switch is closed at $t=0$.
ii.	For the following circuit find R_{th} and hence calculate maximum power

Q	
---	--

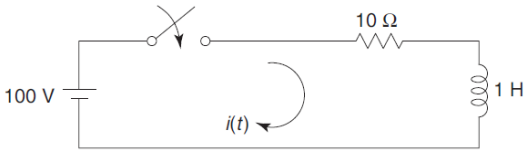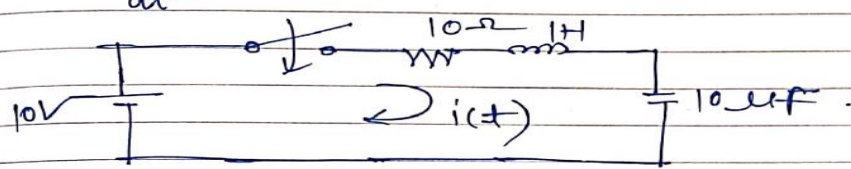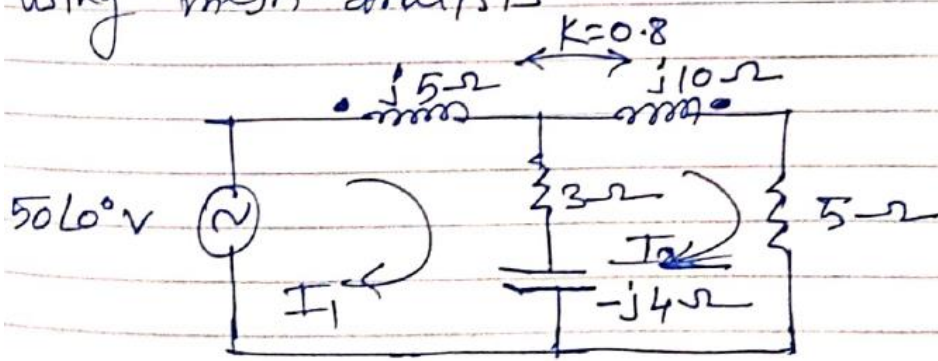3	
A	Solve any Two 5 marks each
i	Test whether the polynomial $P(s)$ is Hurwitz. $P(s) = s^5 + s^3 + s$
ii	For a given network the switch is closed at $t=0$. With zero initial current in the inductor find i, di/dt 
iii	In the network, the switch is closed. Assuming all initial conditions as zero, find i, $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$ 
B	
i	Find the voltage across 5Ω resistor in fig. using mesh analysis 

Obtain Thevenin's equivalent

ii

